
Extending the DAC performance of STM32 microcontrollers

Introduction

Most of the STM32 microcontrollers embed 12-bit DACs (digital to analog converters), specified to operate up to 1 Msp/s (megasamples per second).

Several applications benefit from DACs operating at higher speeds, this note explains how to extend the speed performance of microcontrollers listed in [Table 1](#) using external operational amplifiers (OpAmps).

The STM32 DAC system is described in [Section 1](#) of this document, while an application example focusing on 5 Msp/s sine wave generation is presented in [Section 2](#).

Table 1. Applicable products

Type	Product Series
Microcontrollers	STM32F0 Series
	STM32F1 Series
	STM32F2 Series
	STM32F3 Series
	STM32F4 Series
	STM32F7 Series
	STM32G0 Series
	STM32G4 Series
	STM32H7 Series
	STM32L0 Series
	STM32L1 Series
	STM32L4 Series
	STM32L4+ Series
	STM32L5 Series

Contents

- 1 The STM32 DAC system 5**
 - 1.1 DAC equivalent circuit 5
 - 1.2 DAC speed on the specification 5
 - 1.3 External OpAmp implementation 6
 - 1.4 Digital data update rate 7
 - 1.4.1 DMA double data mode 7
 - 1.5 Summary 8

- 2 Example 9**
 - 2.1 External OpAmp choice 9
 - 2.2 Software implementation 10
 - 2.2.1 Digital sine waveform pattern preparation 10
 - 2.2.2 Setting the sine waveform frequency 10
 - 2.2.3 Offset calibration 11
 - 2.2.4 Output gain calibration 11
 - 2.3 Hardware implementation 14

- 3 Measurements 15**
 - 3.1 Board modification 15
 - 3.2 Measurement results 15

- 4 Conclusions 17**

- 5 Revision history 18**

List of tables

Table 1.	Applicable products	1
Table 2.	Maximum sampling time for different STM32 microcontrollers	8
Table 3.	Example of the offset calibration measurement	11
Table 4.	Example of the calibration measurement	12
Table 5.	Example of digital sample values	12
Table 6.	Component values	14
Table 7.	Document revision history	18

List of figures

Figure 1.	DAC equivalent circuit	5
Figure 2.	External OpAmp configuration	6
Figure 3.	Circuit implementation	14
Figure 4.	Output signal.	15
Figure 5.	FFT result	16

1 The STM32 DAC system

1.1 DAC equivalent circuit


The STM32 microcontrollers, based on Arm^{®(a)} cores, use DACs to transform digital data into analog signals. The DAC can be modeled as a digitally controlled voltage source and an output impedance, as shown in [Figure 1](#).

The output impedance of the DAC is constant, independently from the digital input signal.

When the output buffer is OFF, the DACINT and DACOUT are connected through the resistor R_b , hence the output impedance of the DAC is $R_a + R_b$ (R_b is equal to R_a), and $R_{DAC} = 2 * R_a$ (S1 and S2 switches are open).

When the buffer is enabled, the OpAmp is configured as an inverting amplifier with $A_v = -1$, and the output impedance is almost zero thanks to the feedback loop.

Figure 1. DAC equivalent circuit

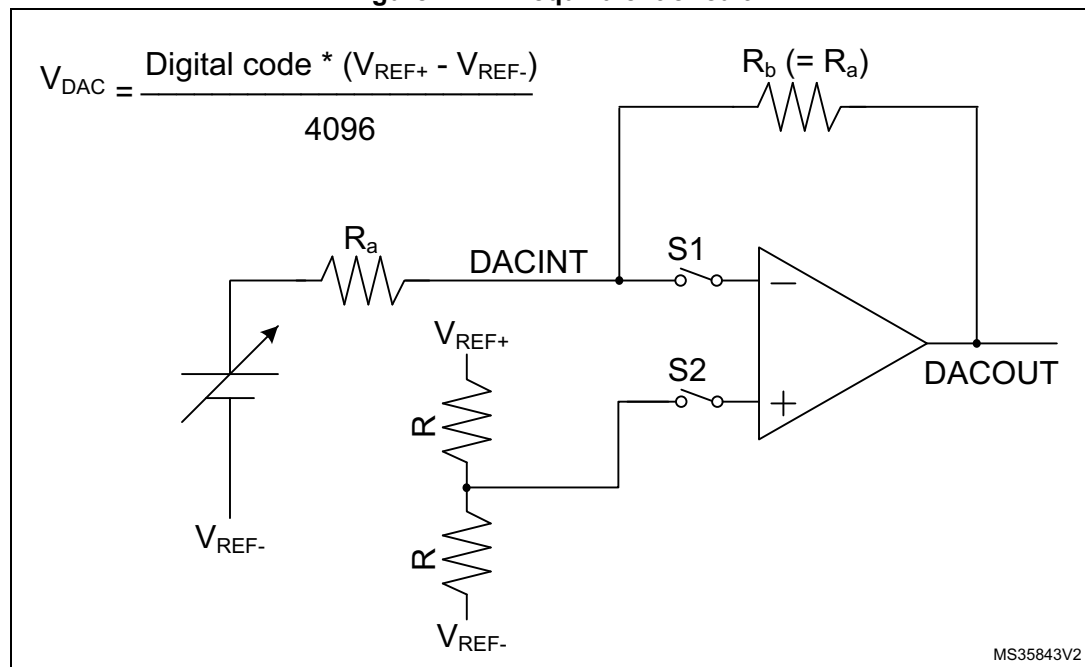

1.2 DAC speed on the specification

When the output buffer is enabled on the DAC output, the speed is specified by the output buffer performance. This number is indicated in the T_{settling} or Update rate in the product datasheet.

arm

a. Arm is a registered trademark of Arm Limited (or its subsidiaries) in the US and/or elsewhere.

When the output buffer is disabled, the output signal speed simply follows the RC constant, which is determined by the DAC output impedance R_{DAC} ($= 2 * R_a$) and the capacitive load on the DACOUT pad.

As an example, the STM32F407 defines the impedance output with buffer off at a maximum value of 15 kΩ. If a 10 pF capacitive load (including the parasitic capacitance of the STM32F407 device on DACOUT pad) is considered, to get ± 1 LSB of the final value (from lowest code to highest code) we have

$$1 - \frac{1}{2^N} = 1 - e^{-T/(CR)}$$

Solving for T gives $T = CR * N * \ln 2 = 0.693 CR * N = 1.8 \mu s$, hence, in this configuration the conversion time cannot be smaller than 1.8 μs (equivalent to a frequency of 555 kHz).


This analysis does not include any effect of the switching speed of the DAC itself and its transient. When using high speed, these factors cannot be ignored, they degrade the performance.

1.3 External OpAmp implementation

As described in [Section 1.2](#), the output DAC conversion time is specified by the embedded output buffer when buffer is enabled. When buffer is disabled, the output impedance and the DACOUT capacitance (C_p) will determine the conversion time.

There is a configuration where it is possible to ignore the DACOUT capacitance. By using external OpAmp in inverting mode, the DACOUT node voltage will be fixed, as shown in [Figure 2](#).

Figure 2. External OpAmp configuration

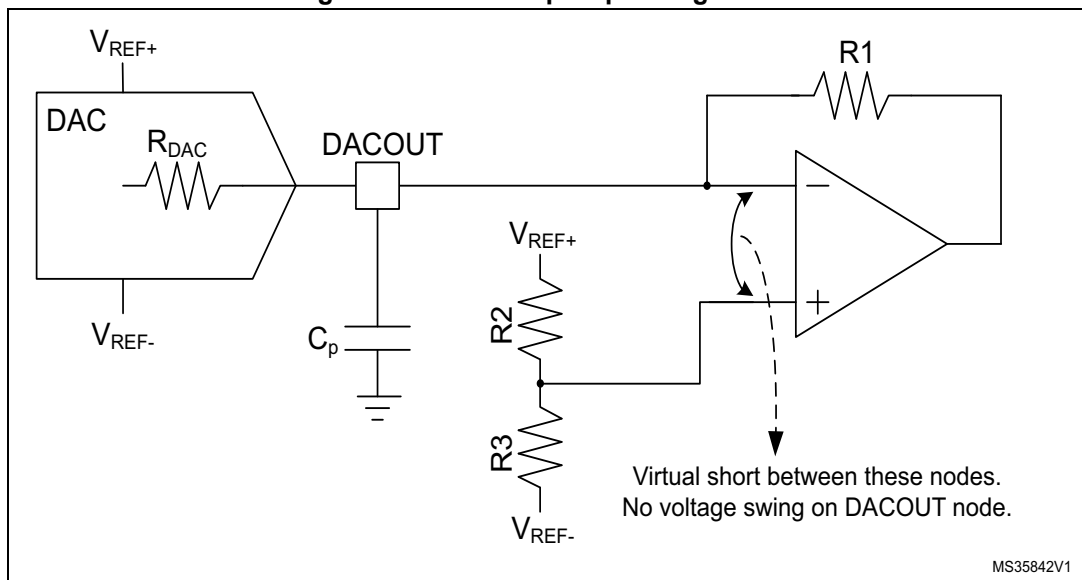

In this configuration there is a minor limitation due to the RC constant, the main limitation being the external OpAmp speed (gain bandwidth and slew rate) and the DAC digital data update rate. There are, however, some disadvantages. The feedback resistor R1 needs to be equal to the R_{DAC} on chip of the STM32, otherwise it will create a DAC gain error.

Integrated resistors usually feature a rather wide spread on their absolute value, and significant variation over temperature, hence it is necessary to calibrate the gain error (discussed in detail in [Section 2.2.4: Output gain calibration](#)).

It is also possible to use the external OpAmp with voltage follower mode. This enhances the output bandwidth and slew rate, however the R_{DAC} output impedance and the parasitic capacitor on the DACOUT form an RC filter that limits the speed performance.

For the voltage follower mode, it is not necessary to perform the gain calibration.

1.4 Digital data update rate

The STM32 DAC output data need to be written to the DAC holding register (DHR), then the data is moved to the DAC output register (DOR) for the conversion.

Generally, the data are saved in a RAM, and the CPU is in charge of the transferring the data from RAM to DAC.

When using the DMA, the overall performance of the system is increased by freeing up the core. This is because data is moved from memory to DAC by DMA, without need for any actions by the CPU. This keeps CPU resources free for other operations.

The trigger of the DAC conversion can be done by the software, external triggers or by the timers. For the high speed conversion cases, it is recommended to use the timer trigger in combination with the data transfer done by the DMA.

The transfer speed from memory to the DAC is limited by several factors, among them:

- the clock cycle of the APB or of the AHB (DAC clock)
- the DMA transfer cycle from memory to the DAC (includes the AHB to APB bridge)
- the trigger mechanism itself.

The DAC on STM32F407x microcontrollers is running on the APB1:

- three cycles after the trigger, DHR data is moved to the DOR register
- at the same time a DMA request is generated from DAC to DMA
- DMA transfer takes at least one APB clock cycle.

So a total of four APB clock cycles is needed to update the DOR data. As APB1 maximum clock is 42 MHz (for ST32F407x), 10.5 Msps is the maximum update rate for the DAC output register when timer trigger and the DMA are used for the data update.

The minimum transfer clock cycle by DMA to the DAC is not the same for all STM32 microcontrollers, because of the different bus configuration.

1.4.1 DMA double data mode

Some DACs on STM32 MCUs support DMA double data mode. When the DMA controller is used in Normal mode, only 8- or 12-bit data are transferred by a DMA request. As the STM32 MCUs can be accessed with 32-bit data bus, DMA double data mode transfers two 12-bit sets data at once, thus requiring lower bus occupation compared to the normal mode.

Table 2 shows the maximum sampling rate for different STM32 products.

Table 2. Maximum sampling time for different STM32 microcontrollers

Product	Max bus speed	DAC max sampling rate
STM32F0 Series	48 MHz	4.8 Msps
STM32F100xx	24 MHz	2.4 Msps
STM32F101xx STM32F103xx STM32F105xx STM32F107xx	36 MHz	4.5 Msps
STM32F2 Series	30 MHz	7.5 Msps
STM32F3 Series	36 MHz	4.5 Msps
STM32F40x STM32F41x	42 MHz	10.5 Msps
STM32F42x	45 MHz	11.25 Msps
STM32F7 Series	54 MHz	13.5 Msps
STM32G0 Series	64 MHz	8.0 Msps
STM32G4 Series	150 MHz	16.67 Msps 30 Msps (DMA double data mode)
STM32H7 Series	100 MHz	18.18 Msps
STM32L0 Series	32 MHz	4.0 Msps
STM32L1 Series	32 MHz	3.2 Msps
STM32L4 Series	80 MHz	10 Msps
STM32L4+ Series	120 MHz	12 Msps
STM32L5 Series	110 MHz	11 Msps

Note: Values reported in Table 2 have been measured on the bench, when bus is not used by any other system: in real applications it is necessary to have some margin.

1.5 Summary

By using an external high speed OpAmp, it is possible to extend the speed performance of the STM32 DACs by more than 1 Msps, see Section 2 for an example showing how to use this technique on STM32 products.

2 Example

The example of the high speed use of the DAC is based on STM32F407, it shows how to generate a 200 kHz sine wave by the DAC operating at 5 Msps.

2.1 External OpAmp choice

As indicated before, the external OpAmp will define the DAC total performance.

To choose the OpAmp, the following parameters must be considered.

- slew Rate
- gain bandwidth (GBW)
- open loop gain
- supply voltage range
- output voltage swing performance
- input common mode voltage range
- minimum stable gain.

In the case of lowest to highest code transient on 5 Msps case with V_{REF} voltage 3.3 V, the OpAmp needs to have a slew rate higher than $3.3 * 5 * 10^6 = 16.5$ Volts/ μ s.

If STM32 DAC operates at 3.3 V, it is possible to use the OpAmp 3.3 V supply (it is also possible to consider another analog supply rail, actually this is the option used in the example).

It is recommended to have at least two times of sampling speed of the gain bandwidth, so, for 5 Msps, GBW needs to be wider than 10 MHz.

To keep good DAC linearity, open loop gain must be higher than 60 dB.

If it is needed to have the output voltage near the supply voltage, then the output voltage swing of the OpAmp must preferably be rail to rail, otherwise, if voltage swing is near to the supply or ground rail, the signal is saturated and this results in distortion.

Even the OpAmp negative input is fixed at the reference voltage level, it is necessary to verify that the input common voltage range covers the reference voltage level with a margin.

The used OpAmp gain is about -1, so the OpAmp must be stable at this gain.

By considering above criteria, LMH6645/6646/6647 from Texas Instruments fit the requirements:

- slew rate: 22 Volts/ μ s;
- gain band width: 55 MHz;
- open loop gain: 87 dB;
- supply voltage range: 2.5 to 12 V;
- input common mode voltage 0.3 V beyond rails;
- output voltage swing 20 mV from rails;
- stable from gain +1.

2.2 Software implementation

For this example the STM32F407 is powered with a 3.3 V supply.

2.2.1 Digital sine waveform pattern preparation

As described in *Audio and waveform generation using the DAC in STM32 microcontrollers* (AN3126), available on www.st.com, a sine wave pattern needs to be prepared according to the following formula

$$Y_{\text{SineDigital}}(x) = \left(\sin\left(2\pi \cdot \frac{x}{n_S}\right) + 1 \right) \cdot \frac{0x\text{FFF} + 1}{2}$$

Digital inputs are converted to output voltages by linear conversion between 0 and $V_{\text{REF+}}$.

The analog output voltage on each DAC channel pin is determined as:

$$\text{DAC}_{\text{Output}} = V_{\text{REF}} \cdot \frac{\text{DOR}}{\text{DAC}_{\text{MaxDigitalValue}}}$$

So the analog sine waveform can be determined by the following equation

$$Y_{\text{SineAnalog}}(x) = 3.3\text{Volt} \cdot Y_{\text{SineDigital}}(x) / 0x\text{FFF}$$

The table can be saved in the memory and transferred by DMA. The transfer is triggered by the same timer that triggers the DAC.

2.2.2 Setting the sine waveform frequency

To set the frequency of the sine wave signal, it is necessary to set the frequency of the timer trigger output. The frequency of the produced sine wave is

$$f_{\text{Sinewave}} = f_{\text{TimerTRGO}} / n_S$$

If TIMx_TRGO is 5 MHz ($n_S=25$), then the frequency of the DAC sine wave is 200 kHz.

To have the exact frequency on the output, system clock need to be adjusted, so that the timer can generate exactly 5 MHz.

In STM32F407 system, some timer can run with a clock frequency twice the one of the APB1 clock, so resolution is two times better than APB1 clock. However DAC will capture the trigger signal by APB1 clock, so the DAC timing cannot be better than APB1 clock.

For example, if the timer is programmed with 25 clock cycles (corresponding to 12.5 cycles of the APB1 clock) then the DAC trigger occurs 12 times, then 13 times, alternately. So one APB1 clock results in jitter on every sampling period.

Here is the example of the clock setting:

- System clock source = PLL (HSE)
- SYSCLK (Hz) = 160000000
- HCLK (Hz) = 160000000
- AHB prescaler = 1
- APB1 prescaler = 4
- APB2 prescaler = 2
- HSE frequency (Hz) = 8000000
- PLL_M = 8
- PLL_N = 320
- PLL_P = 2
- PLL_Q = 7

TIM6 has been used for the trigger.

With this configuration, 80 MHz is the timer clock, so, to get 5 MHz trigger, the prescaler has been set to 1 (PSC = 0) and the counter to 16 (CNT = 15).

2.2.3 Offset calibration

The use of an external OpAmp will introduce additional offsets, among them that of the OpAmp itself, and that coming from the external V_{REF} resistor ladder.

To do the calibration, it is necessary to connect the output of the OpAmp to one of the available ADC channels of the STM32 microcontroller.

The procedure to calibrate the offset is the following one (see [Table 3](#)):

1. set up DAC DOR as 2047
2. measure the OpAmp output by the ADC
3. set up the DAC DOR of the ADC result of last measurement (in this case 2065)
4. verify the result with the ADC (in this case, 2048, still 1LSB offset).

Table 3. Example of the offset calibration measurement

DAC DOR	ADC result value
2047	2065
2065	2048

2.2.4 Output gain calibration

As indicated before, output gain is defined by the ratio of the DAC output impedance and the feedback resistance of the external OpAmp.

The output gain calibration has to be performed during the initialization of chip, and every time the temperature changes significantly (e.g. more than 10 °C). Temperature changes can be detected by the on chip temperature sensor.

To do the calibration connect the output of the OpAmp to one of the available STM32 ADC channels.

Following is the method to calibrate the gain (see [Table 4](#)):

1. set up DAC DOR as 1023
2. measure the OpAmp output by the ADC
3. set up DAC DOR as 3071
4. measure the OpAmp output by the ADC.

Table 4. Example of the calibration measurement

DAC DOR	ADC result value
1023	3135
3071	983

So the amplifier has a gain of 1.0508, obtained as (3135 - 983) / 2048.

This result can be used in the equation shown in [Section 2.2.1](#). It is recommended to have some margin (e.g. 100 mV) for each of the supply rail and ground rails. The digital code swing must be less than 200 mV from the supply, and also use the gain calibration factor

$$Y_{\text{SineDigital}}(x) = \frac{3.1}{3.3 \cdot 1.0508} \cdot \left(\sin\left(2\pi \cdot \frac{x}{n_S}\right) + 1 \right) \cdot \frac{0x\text{FFF} + 1}{2} + 18$$

By using the above equation, [Table 5](#) can be generated.

Table 5. Example of digital sample values

Sample	Digital sample value $Y_{\text{SineDigital}}(x)$
0	2066
1	2521
2	2948
3	3319
4	3612
5	3807
6	3893
7	3864
8	3723
9	3477
10	3142
11	2740
12	2295
13	1837
14	1392
15	990
16	655

Table 5. Example of digital sample values (continued)

Sample	Digital sample value $Y_{\text{SineDigital}} (x)$
17	409
18	268
19	239
20	325
21	520
22	813
23	1184
24	1611

Note: The output signal is inverted compare to the digital code, due to the inverting amplifier stage of the external OpAmp.

2.3 Hardware implementation

As described in [Section 2.1](#), an external component has been chosen.

The actual circuit is shown in [Figure 3](#), the component values are listed in [Table 6](#).

R1, chosen as typical output DAC impedance, is 12.5 kΩ (for other devices, consult the electrical specification in the datasheet). C1 is added to avoid overshoot on the output signal.

Figure 3. Circuit implementation

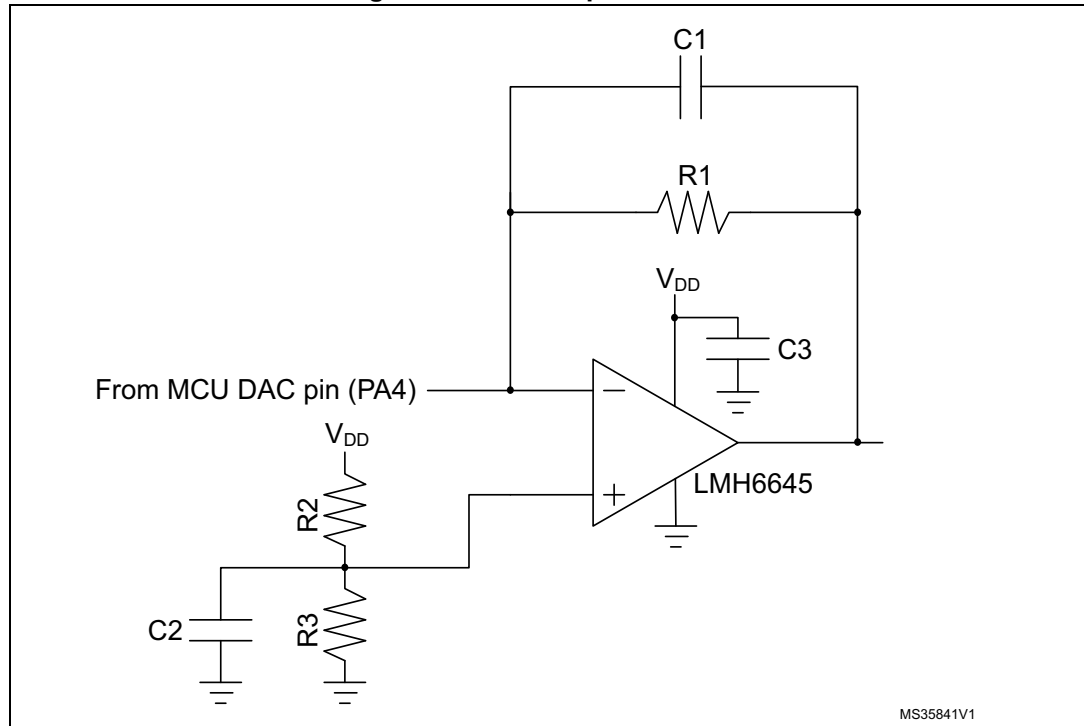


Table 6. Component values

Type	Component	Value
Resistor	R1	12 kΩ
	R2	10 kΩ
	R3	10 kΩ
Capacitor	C1	5 pF
	C2	100 nF
	C3	100 nF

3 Measurements

The measurements have been done on a STM32F4Discovery board with the configuration shown in [Figure 3](#).


3.1 Board modification

STM32F407 DAC1 output is assigned to PA4, which, in turn, is connected to the on-board audio codec through a 100 kΩ resistor to GND. To remove this effect, the R48 (0 Ω) resistor has been removed from the board.

3.2 Measurement results


The output signal is shown in [Figure 4](#), while [Figure 5](#) is the corresponding FFT analysis.

Figure 4. Output signal

 

Output swing is not equal to 3.1 V_{pp}, as sampling time is not aligned with the peak of the sine wave signal.

Figure 5. FFT result

 

The second and third harmonics are around the noise level.

4 Conclusions

The DAC used by STM32F4 microcontrollers has been characterized up to 1 Msps: by using high speed external OpAmp, it can operate up to 5 Msps.

Additional remarks:

- by using high speed sampling rate, it is possible to reduce the anti-aliasing filter order
- by using the on chip ADC, it is possible to calibrate the output swing and the offset.

5 Revision history

Table 7. Document revision history

Date	Revision	Changes
03-Nov-2014	1	Initial release.
02-Aug-2015	2	Added STM32L4 Series in Table 1: Applicable products and in Table 2: Maximum sampling time for different STM32 microcontrollers .
19-Sep-2019	3	Document scope extended to STM32L4+, STM32L5, STM32H7, STM32G0 and STM32G4 Series, hence updated Table 1: Applicable products and Table 2: Maximum sampling time for different STM32 microcontrollers . Updated Section 1.1: DAC equivalent circuit , Section 1.3: External OpAmp implementation and Section 2.2.4: Output gain calibration . Added Section 1.4.1: DMA double data mode . Updated Figure 1: DAC equivalent circuit . Minor text edits across the whole document.

IMPORTANT NOTICE – PLEASE READ CAREFULLY

STMicroelectronics NV and its subsidiaries (“ST”) reserve the right to make changes, corrections, enhancements, modifications, and improvements to ST products and/or to this document at any time without notice. Purchasers should obtain the latest relevant information on ST products before placing orders. ST products are sold pursuant to ST’s terms and conditions of sale in place at the time of order acknowledgement.

Purchasers are solely responsible for the choice, selection, and use of ST products and ST assumes no liability for application assistance or the design of Purchasers’ products.

No license, express or implied, to any intellectual property right is granted by ST herein.

Resale of ST products with provisions different from the information set forth herein shall void any warranty granted by ST for such product.

ST and the ST logo are trademarks of ST. For additional information about ST trademarks, please refer to www.st.com/trademarks. All other product or service names are the property of their respective owners.

Information in this document supersedes and replaces information previously supplied in any prior versions of this document.

© 2019 STMicroelectronics – All rights reserved