

## Using low voltage precision op amps for a high voltage sensing application

Nicolas AUPETIT  
Application engineer, STMicroelectronics

August 15<sup>th</sup>, 2016

### Introduction

Dedicated devices that support extended common mode voltage are generally used for high side current sensing. But dedicated devices have their own limitations. What about when the common mode voltage exceeds 100V? Is it possible to precisely measure a current then? A classic 5V op amp seems totally inappropriate for this kind of measurement. But with just a few external components, we are going to see that low voltage amplifiers are absolutely appropriate for sensing a current accurately without any of the common mode voltage limitations.

### Schematic & description

The main goal of this application is to measure the current of an industrial motor control, powered with 150V, as illustrated by figure 1, thanks to a shunt resistor. In order to get a precise measurement for low current, a 5V precision op amp is used.

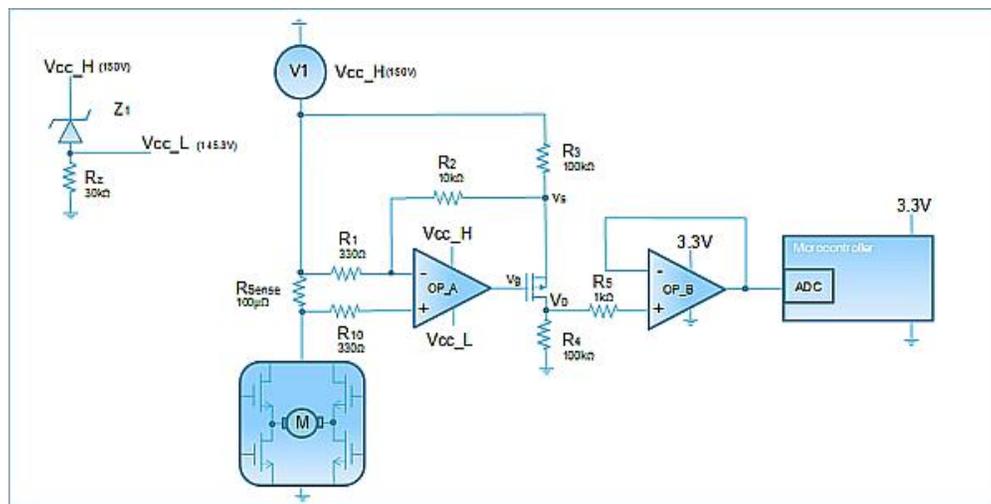


Figure 1: Typical application

Won't 150V input burn up the op amp? Not if the V1 voltage is used to generate the positive power supply (Vcc\_H) for the first op amp, OP\_A.

If we use a Zener diode (BZT52C4V7S) with a 4.7V breakdown voltage, the negative power supply (Vcc\_L) of the OP\_A is generated. In this way, the OP\_A is powered with 4.7V, from Vcc\_L=145.3V to Vcc\_H=150V.

The resistance Rz is used to bias the zener diode (~5mA) and provide a return path for the bias current of the op amp (~40µA).

The voltage, Vsense, is the result of the current flowing through Rsense, and it is amplified by R1, R2, R3 and R4 resistances.

The P-MOSFET (BSP2220) sources an accurate output current proportional to the current flowing into  $R_{sense}$ , and with the  $R4$  resistance, it generates a voltage  $V_o$  with respect to ground, which is proportional to the high side current. The voltage output of the first stage can be given by equation 1:

$$V_o = \frac{V_{sense} R4}{R1 R3} \cdot (R1 + R2 + R3) \quad (1)$$

The second op amp, OP\_B, is necessary to buffer  $V_o$  voltage. A  $R5$  resistance may be added in order to protect the intrinsic ESD diode of the OP\_B in case of a high current that might flow in the input pins at start up.

The maximum current drawn by the motor control is 100A. So with a  $100\mu\Omega$  shunt resistor, the maximum  $V_{sense}$  is 10mV. The maximum output voltage is dependent on  $V_{sense}$  voltage, and the resulting output current across  $R4$ . And as it is treated by an ADC of the microcontroller, this maximum output voltage  $V_o$  must not exceed 3.3V.

The values of the components must be chosen carefully to make the system work properly. The main goal is to work with a low  $|V_{gs}|$  in order to not saturate the output of OP\_A.

Because keeping a low current  $I_{ds}$  helps, we choose a high value for  $R4$ .

And in order to avoid any saturation of the output of the op amp, the gain relative to the op amp OP\_A, given by the ratio  $R2/R1$ , should not be too high.

We have to compromise in the choice of components' values, which must follow equation 2:

$$|V_{gs \max}| < V_{zener} - \frac{R3 \cdot (R1 + R2)}{R4 \cdot (R1 + R2 + R3)} \cdot V_{o\_max} \quad (2)$$

- Where  $V_{gmax}$  is the  $V_{gs}$  needed to allow a current into the transistor of  $I_{dmax} = V_{o\_max}/R4$
- And  $V_{zener} = V_{cc\_H} - V_{cc\_L}$

Let's now have a look to the precision of such a system. The inaccuracy is mainly due to the mismatch of the resistances as well as the offset of amplifiers.

### Impact of the mismatch of the resistances

Equation 1 gave the result of the output voltage by considering that the resistances used are perfectly matched. Unfortunately, this is not the case, as the resistances have their own precision.

The error done on the gain, due to the mismatch of the resistances is given by the following formula:

$$V_o = \frac{I_{sense} \cdot R_{shunt}}{R1} \cdot \frac{R4}{R3} \cdot (R1 + R2 + R3) \cdot \left[ 1 + \left( \frac{2R1 + 4R2 + 2R3}{R1 + R2 + R3} \right) \cdot \epsilon\alpha + \epsilon R_{shunt} \right] \quad (3)$$

- Where  $\epsilon\alpha$  is the precision of any of the resistances, and  $\epsilon R_{shunt}$  is the accuracy of the shunt resistor.

From equation 3, we can see that the  $R2$  resistance has a bigger impact on the error than the other resistances. And so its value must be chosen to be as low as possible ( $10k\Omega$ ). Note also that the sum of  $R1$  and  $R3$  should be high and unbalanced in order to achieve the gain, with  $R1$  ideally low to limit the noise.

## Impact of the Vio

Another error must be taken into consideration: the input voltage offset. In this application, we have chosen the TSZ121, a chopper amplifier, because it exhibits a very low  $V_{io}$ ,  $8\mu\text{V}$  over temperature. This error becomes predominant especially when very small current has to be measured. The transfer function taken into account the  $V_{io}$  can be written as follows:

$$V_{out} = \frac{(V_{sense} \pm V_{io1})}{R_1} \cdot \frac{R_4}{R_3} \cdot (R_1 + R_2 + R_3) \pm V_{io2} \quad (4)$$

Where  $V_{io1}$  is the input offset of the first op amp (OP\_A), and  $V_{io2}$  is the input offset of the second op amp (OP1\_B). As the TSZ121 has an extremely low input offset voltage,  $V_{io2}$  can be neglected.

In order to have an idea of the total error on the output, we add the mismatch of the resistances and the offset of the op amp. Finally, the output voltage can be written as equation 5:

$$V_O = \frac{(I_{sense} \cdot R_{shunt})}{R_1} \cdot \frac{R_4}{R_3} \cdot (R_1 + R_2 + R_3) \cdot \left[ 1 + \left( \frac{2R_1 + 4R_2 + 2R_3}{R_1 + R_2 + R_3} \right) \cdot \epsilon\alpha + \epsilon R_{shunt} \right] \pm \frac{V_{io}}{R_1} \cdot \frac{R_4}{R_3} \cdot (R_1 + R_2 + R_3) \quad (5)$$

The graphs in figures 2 and 3 represent the maximum error expected over temperature, by taking into account the shunt accuracy.

**Total error on output over temperature  
with 1% precision resistances and Rshunt 1%**


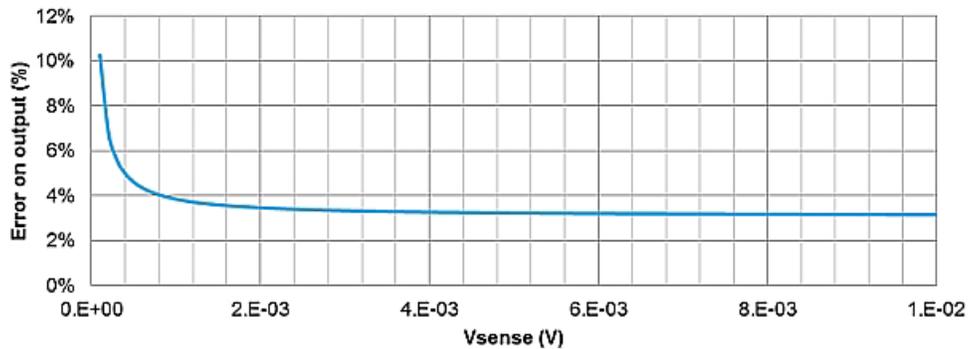


Figure 2: Total error assuming 1% resistances with Rshunt 1%

**Total error on output over temperature  
with 0.1% precision resistances and Rshunt 1%**

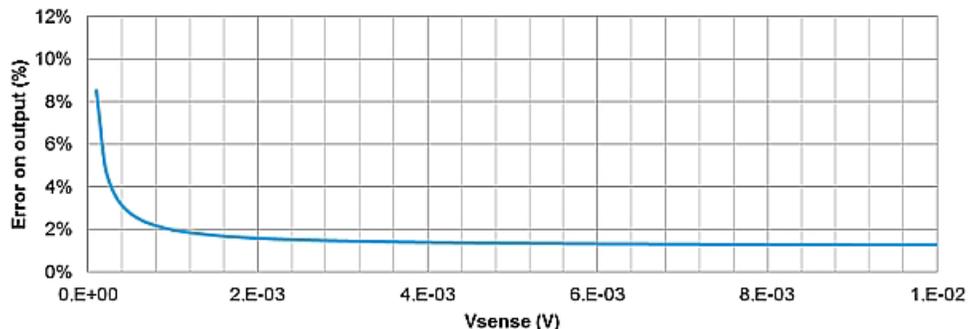

*Figure 3: Total error assuming 0.1% resistances with Rshunt 1%*

### **Conclusion**

Dedicated amplifiers are commonly used to realize high side current sensing measurement. But in applications where the common mode is higher than 70V, we've seen that this kind of measurement should be done with a conventional 5V op amp.

We've shown that high side current sensing can be achieved using a precision op amp such as the TSZ121 amplifier, combined with a zener diode in order to work in a 5V range and level shift transistor.

We've taken some errors due to the resistances and amplifiers used into account. We advise using 0.1% precision resistances to obtain a good accuracy for the current measurement.